

ESERCIZI DI ELETTRICITÀ E
MAGNETISMO

FOGLIO 24-47

1, 3, 4, 8, 7


1 | $\Sigma = 0,1 \text{ m}^2$, $h = 1 \text{ cm}$, $\Delta V = 1000 \text{ V}$

$\epsilon_{v_1} = 3$ $\epsilon_{v_2} = 5$ $\epsilon(z) = \epsilon_{v_1} - z(\epsilon_{v_1} - \epsilon_{v_2})$

NEL VUOTO

$$\begin{cases} C_0 = \epsilon_0 \frac{\Sigma}{h} = 8,85 \cdot 10^{-11} \text{ F} \\ q_0 = C_0 \Delta V = 8,85 \cdot 10^{-8} \text{ C} \end{cases}$$

$$\sigma_0 = \frac{q_0}{\Sigma} =$$

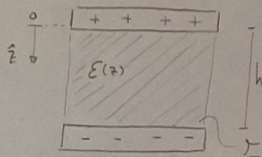

[2] $\vec{E}_0$, $E_0 = 200 \text{ V/m}$ $\epsilon_v = 4$ $\theta_0 = 30^\circ$

USO IL FATTO $D_m = \cos \theta = \epsilon E_m$

$$\epsilon_v E_m = \epsilon_v E_{0m} ; \epsilon_v E \cos \theta_1 = \epsilon_v E_0 \cos \theta_0$$

PERÒ SO $E_t = \cos \theta \rightarrow E \sin \theta_1 = E_0 \sin \theta_0$


$$\Rightarrow \epsilon_v E_0 \frac{\sin \theta_0}{\sin \theta_1} \cos \theta_1 = \epsilon_v E_0 \cos \theta_0 ; \left| \frac{\epsilon_v}{\epsilon_v} = \frac{\tan \theta_1}{\tan \theta_0} \right| \Rightarrow \theta_1 = \tan^{-1} \left(\frac{\epsilon_v \tan \theta_0}{\epsilon_v} \right) = 66,98^\circ$$

$$\cos \epsilon_v E \cos \theta_1 = \epsilon_v E_0 \cos \theta_0 \Rightarrow E = \frac{E_0 \cos \theta_0}{\epsilon_v \cos \theta_1} = 108,9 \text{ V/m}$$


$$\vec{P} = \epsilon_0 (\epsilon_v - 1) \vec{E} \Rightarrow |P| = 2,89 \cdot 10^{-9} \text{ V/m}$$

$$\sigma_p = \vec{P} \cdot \hat{n} = P \cos \theta_1 = 1,15 \cdot 10^{-9} \text{ C/m}^2$$

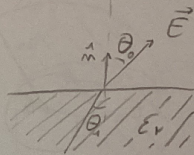SEGNO NEGATIVO ESCE SE $\vec{E}_0$
 ENTRANTE IN $\epsilon_v \cos \theta_1$
 $E_m = -E_0 \cos \theta_0$



3

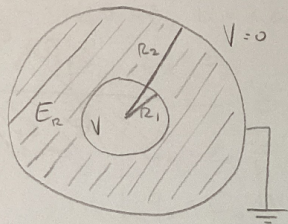

RIGIDITÀ DIELETTICA È IL VALORE DI CAMPO
ELETTICO MASSIMO APPLICABILE PRIMA DELLE
SCARICHE

QUINDI DEVE SEMPRE VALERE

$$E < E_r$$


$$V < V_r = E_r \cdot R_2$$

SONO NEL VUOTO, SO $C_0 = 4\pi\epsilon_0 \frac{R_1 R_2}{R_2 - R_1}$

$$V_1 - V_2 = V = \frac{q}{4\pi\epsilon_0} \left(\frac{1}{R_1} - \frac{1}{R_2} \right) = \frac{q}{4\pi\epsilon_0} \frac{R_2 - R_1}{R_1 R_2}$$

IN UN DIELETTICO SO

$$V_k = \frac{V_0}{E_r}$$

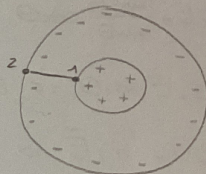

4) $\rho = 2 \Omega m$, $d = 2 cm$, $a = 2 mm$, $b = 5 mm$, $V = 20 V$

1) CASO $\hat{n} // ALL'ASSE$


$$\tau = \pi(b^2 - a^2) \quad , \quad \tau = \pi d(b^2 - a^2)$$

CALCOLO $R = \rho \frac{d}{\tau} = 606,3 \Omega$

$$\hat{n} = \frac{V}{R} = 0,033 A$$

$$P = V \hat{n} = 0,66 W$$
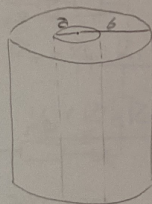
$$Z \Rightarrow \hat{j} = \frac{\hat{n}}{\tau} = 500,2 \frac{A}{m^2}$$



2) CASO $\hat{n}$ RADIALE


$$R = \int \frac{\rho dr}{\pi(r^2 - a^2)} = \frac{\rho}{\pi} \ln \frac{b^2}{a^2}$$

$$R = \frac{\rho}{\pi} \ln \frac{b^2}{a^2} = 1,23 \Omega$$


$$R = \frac{\rho}{\pi} \ln \frac{b^2}{a^2} = 1,23 \Omega$$

$$R = \frac{\rho}{\pi} \ln \frac{b^2}{a^2} = 1,23 \Omega$$

5

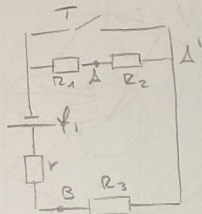


SE T APERTO HO

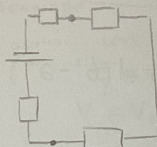

$$R_{23} = R_2 + R_3$$

$$R_{1v} = R_1 + r$$

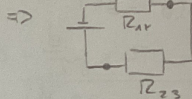

È UN PARTITORE

RESISTIVO

E VOGLIO

$$V_{R_{23}} = V_{AB}$$

$$I_{TOT} = \frac{V}{R_{1v} + R_{23}}$$

$$V_{R_{23}} = R_{23} I_{TOT}$$

$$= V_{AB} = \frac{V}{r + R_2 + R_3 + R_1} (R_2 + R_3)$$


SE T CHIUSO

NEL RAMO DI

R_1, R_2

NON PASSA

CORRENTE

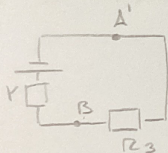

HO

DI

NUOVO

UN



PARTITORE

DI TENSIONE

$$I_{TOT} = \frac{V}{r + R_3}$$

$$V_{R_3} = V_{A'B} = I_{TOT} R_3 = \frac{V}{r + R_3} R_3$$

6

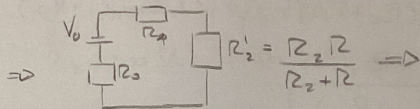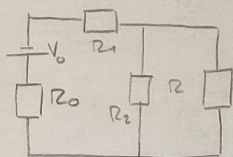

$$R_T = R_0 + R_1 + \frac{R_2 R}{R_2 + R}$$

$$i_T = \frac{V_0}{R_T} = \frac{V_0 (R_2 + R)}{R_0 R_2 + R R_0 + R_1 R_2 + R_2 R + R_1 R_2} = \frac{V_0 (R_2 + R)}{\alpha}$$

$$P = i_T^2 V = \frac{V_0^2 (R_2 + R)}{(R_2 + R)(R_0 + R_1) + R_2 R} = \frac{V_0^2 (R_2 + R)}{\alpha}$$

$$\frac{\partial P}{\partial R} = \frac{V_0^2 R_2}{\alpha^2} + \left(-V_0^2 R_2 R \frac{R_0 + R_1 + R_2}{\alpha^3} \right) = 0$$

$$\frac{V_0^2 R_2}{\alpha^2} = \frac{V_0^2 R_2 R (R_0 + R_1 + R_2)}{\alpha^3} \rightarrow \alpha = (R_2 + R)(R_0 + R_1) + R_2 R = R(R_0 + R_1 + R_2)$$

$$i_T = \frac{V_0}{R_T} = \frac{V_0}{R_0 + R_1 + \frac{R_2 R}{R_2 + R}} \rightarrow V_R = i_T R_2 = \frac{V_0 (R_2 + R)}{(R_2 + R)(R_0 + R_1) + R_2 R} \frac{R_2 R}{R_2 + R} = \frac{V_0 R_2 R}{\alpha}$$

$$P = i_R^2 R = \left(\frac{V_R}{R} \right)^2 R = \frac{V_R^2}{R} = \frac{V_0^2 R_2^2 R}{\alpha^2}$$


$$\frac{\partial P}{\partial R} = \frac{V_0^2 R_2^2}{\alpha^2} + \left(-V_0^2 R_2^2 R \frac{R_0 + R_1 + R_2}{\alpha^3} \right) = 0$$

$$\frac{V_0^2 R_2^2}{\alpha^2} = 2 \frac{V_0^2 R_2^2}{\alpha^3} R (R_0 + R_1 + R_2) \rightarrow \alpha^2 = 2 R (R_0 + R_1 + R_2)$$

$$[R(R_0 + R_1 + R_2) + R_2(R_0 + R_1)]^2 = 2R(R_0 + R_1 + R_2)$$

$$-R(R_0 + R_1 + R_2) = -R_2(R_0 + R_1)$$
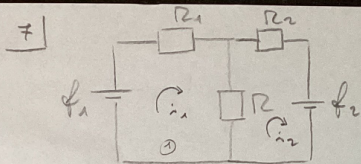
$$\Rightarrow R = \frac{R_2(R_0 + R_1)}{R_0 + R_1 + R_2}$$



$$f_1 = 10V$$

$$R_2 = 200\Omega$$

$$f_2 = 20V$$

$$R = 300$$

$$R_1 = 100\Omega$$

$$\begin{cases} \dot{i}_1(R_1 + R) - \dot{i}_2 R_2 = f_1 \\ \dot{i}_2(R + R_2) - \dot{i}_1 R_1 = -f_2 \end{cases}$$

$$\begin{cases} \dot{i}_1 = \frac{f_1 + \dot{i}_2 R_2}{R_1 + R} \\ \dot{i}_2(R + R_2) - \frac{f_1 + \dot{i}_2 R_2}{R_1 + R} R_1 = -f_2 \end{cases}$$

$$\dot{i}_2(R + R_2)(R + R_1) - (f_1 + \dot{i}_2 R_2)R_1 = -f_2(R_1 + R)$$


$$\dot{i}_2(R + R_2)(R + R_1) - \dot{i}_2 R_1 R_2 = -f_2(R_1 + R) + f_1 R_1$$

$$\dot{i}_2 = \frac{f_1 R_1 - f_2(R_1 + R)}{(R + R_2)(R + R_1) - R_1 R_2} = -0,039A$$

$$\dot{i}_1 = \frac{f_1 + \dot{i}_2 R_2}{R_1 + R} = 5,5 \cdot 10^{-3} A = 0,0055 A$$

8 | $L = 26,7 \text{ km}$ $m_p = 1,67 \cdot 10^{-27} \text{ kg}$ PROTONI $t_0 = 25 \text{ ms}$ $v \approx c$
 $r = 16 \mu\text{m}$
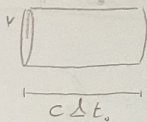
$$I = \pi r^2 = 8 \cdot 10^{-10} \text{ m}^2$$



$$\dot{\lambda} = \frac{dq}{dt_0} = \frac{dq}{dt}$$

$$\Delta q = m_p e \tau = m_p e c \Delta t_0 d\tau$$

$$\Rightarrow d\lambda = \frac{\Delta q}{\Delta t_0} = m_p e c d\tau$$

$$\Rightarrow \dot{\lambda} = m_p e c \pi v^2 = 4,4 \cdot 10^{-9} \text{ A}$$